

# BME2322 – Logic Design

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN

[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)


<https://avesis.yildiz.edu.tr/nakkan>

# LECTURE 6

# Combinational Circuit Design

- Up to now, we have learned all the prerequisite material:
  - Truth tables and Boolean expressions can be used to describe functions
  - Expressions can be converted into hardware circuits (Gates)
  - Boolean algebra and K-maps help simplify expressions and circuits
- Now, we can put all of these foundations to good use, to analyze and design some larger circuits
- Logic circuits for digital systems may be
  - **Combinational** or **Sequential**
- A **combinational circuit** consists of logic gates whose outputs at any time are determined by the current input values, i.e., it has no memory elements
- A **sequential circuit** consists of logic gates whose outputs at any time are determined by the current input values as well as the past input values, i.e., it has memory elements

# Combinational Circuit Diagram

 

- Each input and output variable is a binary variable
- $2^n$  possible binary input combinations
- One possible binary value at the output for each input combination
- A truth table or  $m$  Boolean functions can be used to specify input-output relation


# Design Procedure

1. Specification
  - Write a specification for the circuit if one is not already available
2. Formulation
  - Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
  - Apply hierarchical design if appropriate
3. Optimization
  - Apply 2-level and multiple-level optimization bu using Algebraic or K-map optimization
  - Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters
4. Technology Mapping
  - Map the logic diagram or netlist to the implementation technology selected
5. Verification
  - Verify the correctness of the final design manually or using simulation

# Example – Comparing 2-bit Numbers
 
## Specification for 2-bit comparator

- Let's design a circuit that compares two 2-bit numbers, A and B. The circuit should have three outputs:
  - G ("Greater") should be 1 only when  $A > B$
  - E ("Equal") should be 1 only when  $A = B$
  - L ("Lesser") should be 1 only when  $A < B$
- Make sure you understand the problem
  - Inputs A and B will be 00, 01, 10, or 11 (0, 1, 2 or 3 in decimal)
  - For any inputs A and B, exactly one of the three outputs will be 1
- Two 2-bit numbers means a total of four inputs
  - We should name each of them
  - Let's say the first number consists of digits A1 and A0 from left to right, and the second number is B1 and B0
- The problem specifies three outputs: G, E and L



# Comparing 2-bit Numbers cont.

## Formulation for 2-bit comparator

- To start with filling the truth table is a good way for problem solving. By this way, the relationship ( $>$ ,  $=$ ,  $<$ ) between the inputs (A and B) can be explicitly shown
- A four-input function has a sixteen-row truth table
- It's usually clearest to put the truth table rows in binary numeric order; in this case, from 0000 to 1111 for A1, A0, B1 and B0
- Example:  $01 < 10$ , so the sixth row of the truth table (corresponding to inputs A=01 and B=10) shows that output L=1, while G and E are both 0.

A1	A0	B1	B0	G	E	L
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0	0	0	1
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

# Comparing 2-bit Numbers cont.

- The complete truth table

A1	A0	B1	B0	G	E	L
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0



# Comparing 2-bit Numbers cont.

## Optimization for 2-bit comparator

Let's use K-maps. There are **three** functions (each with the same inputs A1 A0 B1 B0), so we need **three** K-maps

		B1				
		0	0	0	0	
		1	0	0	0	
		1	1	0	1	A0
A1		1	1	0	0	
		B0				

$$G(A1, A0, B1, B0) =$$

$$A1 A0 B0' +$$

$$A0 B1' B0' +$$

$$A1 B1'$$

		B1				
		1	0	0	0	
		0	1	0	0	
		0	0	1	0	A0
A1		0	0	0	1	
		B0				

$$E(A1, A0, B1, B0) =$$

$$A1' A0' B1' B0' +$$

$$A1' A0 B1' B0 +$$

$$A1 A0 B1 B0 +$$

$$A1 A0' B1 B0'$$

																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					</
--	--	--	--	----

$$L(A1, A0, B1, B0) =$$


$$A1' A0' B0 +$$

$$A0' B1 B0 +$$

$$A1' B1$$

# Comparing 2-bit Numbers cont.

Logic diagram for 2-bit comparator

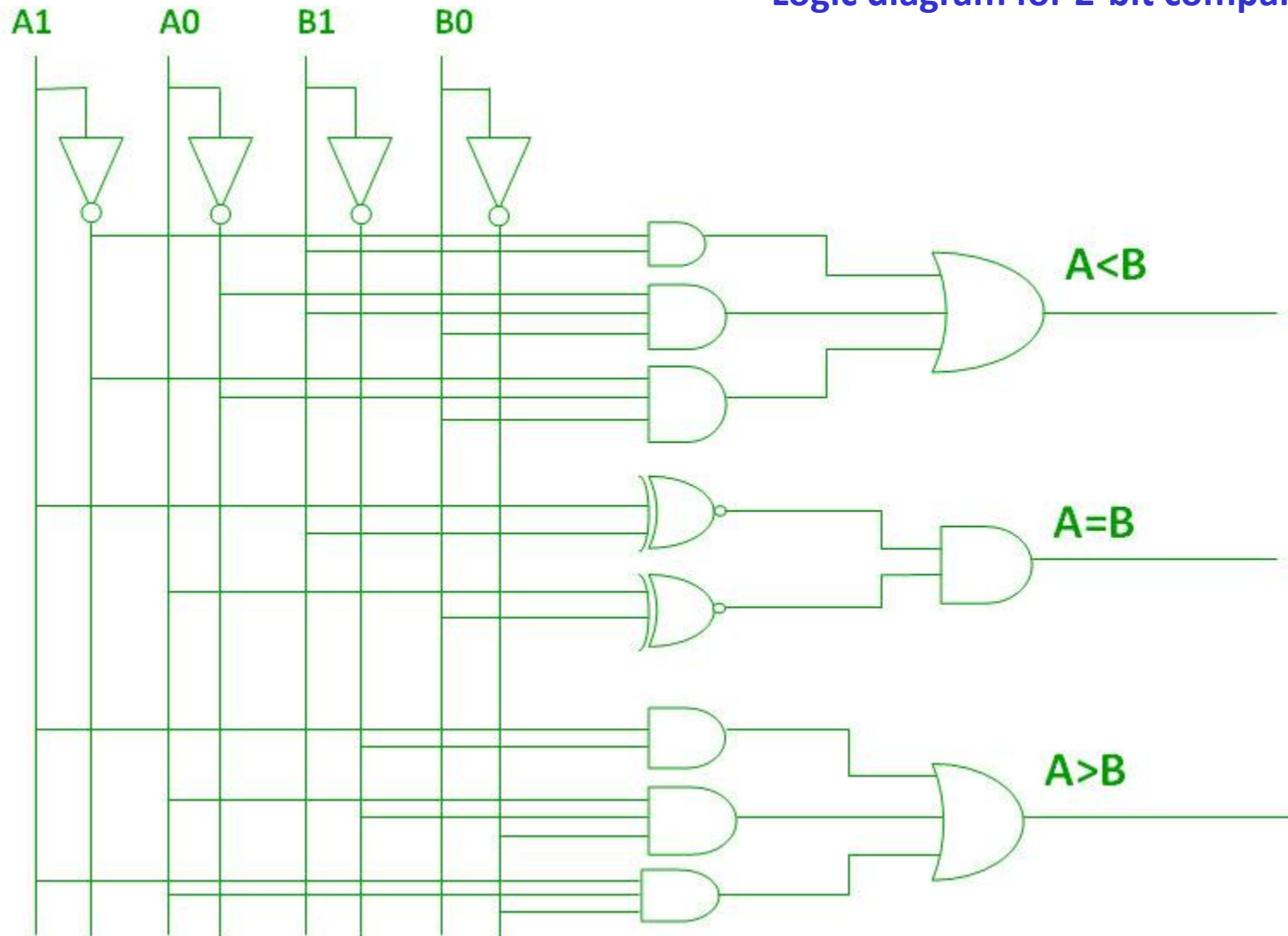


# Technology Mapping

## Mapping Procedures


- To NAND gates
  - To NOR gates
- 
- Some implementation technology usually has a library with only one type of gate (such as 3-input NOR, or 3-input NAND)
  - Technology mapping is a transformation of Boolean expressions into a logic schematic containing only given type(s) of gate(s)
  - The mapping is accomplished by:
    - Replacing AND and OR symbols,
    - Pushing inverters through circuit fan-out points,
    - Canceling inverter pairs

# NAND Mapping Algorithm

1. Replace ANDs and ORs:

 


 2. Repeat the following pair of actions until there is at most one inverter between :
  - a. A circuit input or driving NAND gate output, and
  - b. The attached NAND gate inputs.




# NAND Mapping Example

 
Example -  $F = AB + (AB)'C + (AB)'D' + E$




(a)

 

(b)

 


(c)

 

(d)

# NOR Mapping Example

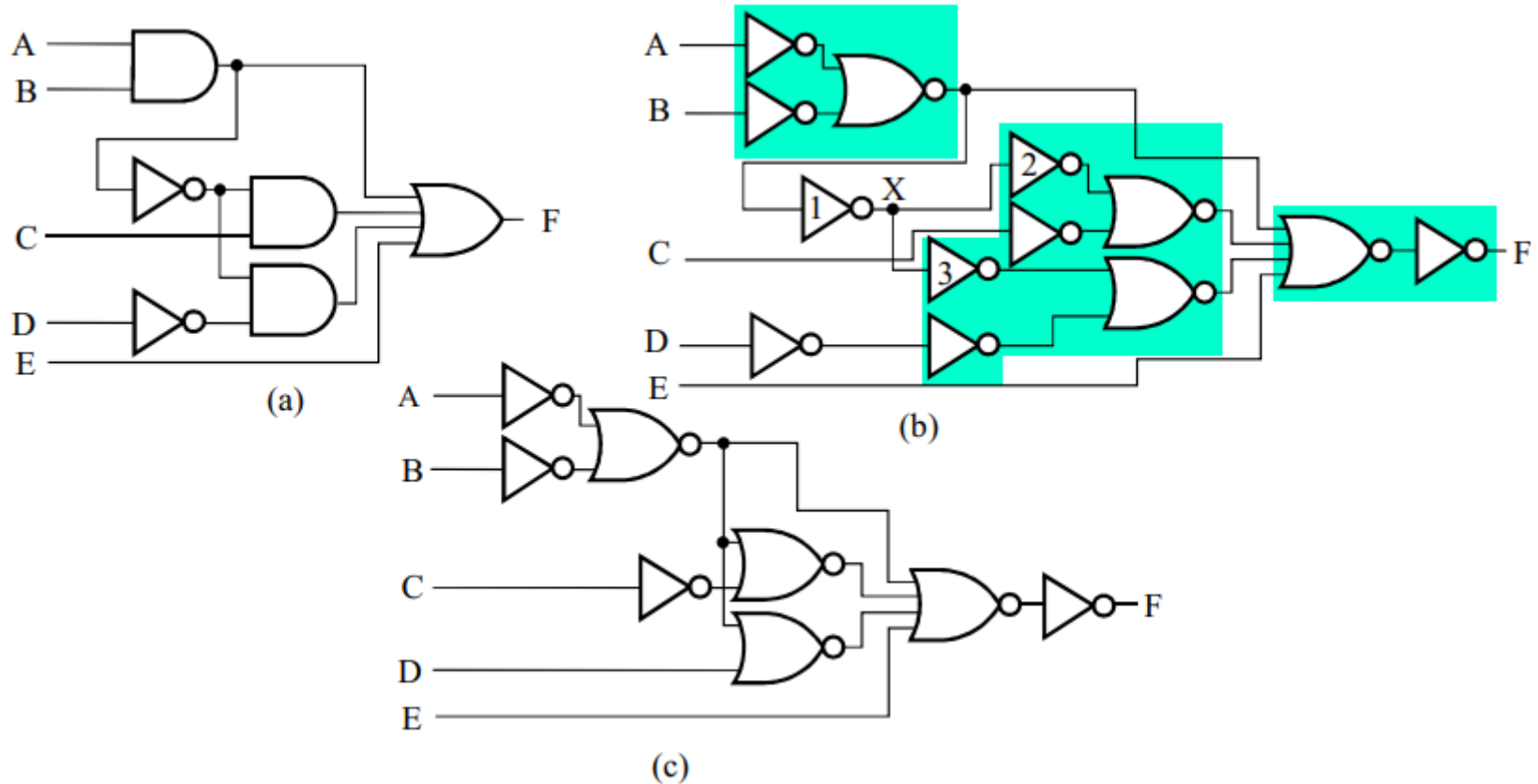Example -  $F = AB + (AB)'C + (AB)'D' + E$



# Verification

- **Verification** - show that the final circuit designed implements the original specification
- Simple specifications are:
  - truth tables
  - Boolean equations
  - HDL code
- **Manual Logic Analysis**
  - Find the truth table or Boolean equations for the final circuit
  - Compare the final circuit truth table with the specified truth table, or
  - Show that the Boolean equations for the final circuit are equal to the specified Boolean equations
- **Simulation**
  - Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.

# Top-Down versus Bottom-Up


- A **top-down** design proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- A **bottom-up** design starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- Much of the material in this course is devoted to learning about combinational blocks used in top-down design.




# Beginning Hierarchical Design

- A single very large-scale integrated (VLSI) processors circuit contains several tens of millions of gates!
- Imagine interconnecting these gates to form the processor
- No complex circuit can be designed simply by interconnecting gates one at a time
- **Divide and Conquer** approach is used to deal with the complexity
  - Break up the circuit into pieces (blocks)
  - Define the functions and the interfaces of each block such that the circuit formed by interconnecting the blocks obeys the original circuit specification
  - If a block is still too large and complex to be designed as a single entity, it can be broken into smaller blocks
  - Any block not decomposed is called a primitive block
  - The collection of all blocks including the decomposed ones is a hierarchy

# Hierarchy for Parity Tree Example

 


(a) Symbol for circuit

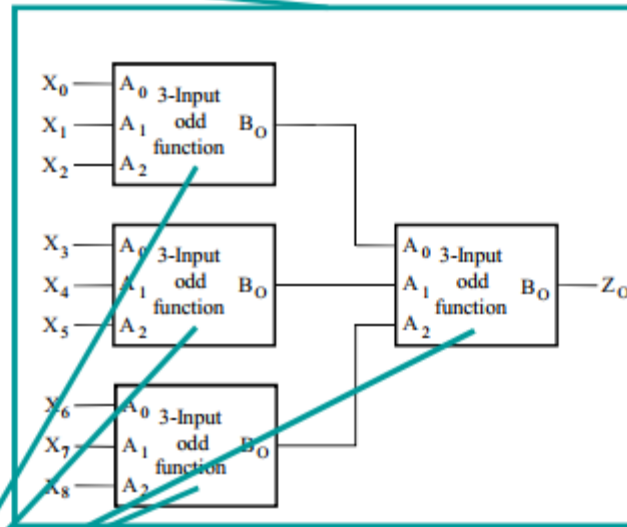

(b) Circuit as interconnected 3-input odd function blocks



 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



(d) Exclusive-OR block as interconnected NANDs

# Designing Complex Circuits


- Computer-Aided Design (CAD) tools
  - Schematic capture tools: Support the drawing of blocks and interconnections at all levels of the hierarchy
  - Libraries of graphic symbols
  - Logic Simulator
- Hardware Description Languages (HDLs)
  - VHDL and Verilog, both are the IEEE standard
  - VHDL: Very High Speed Integrated Circuits (VHSIC) HDL
  - Like programming languages, but tuned to describe hardware structures and behaviour
  - Alternative to schematics (structural description)
  - Behavioural description also possible
  - Logic synthesis: Register Transfer Level (RTL) of a system -> Netlist (structural description)

# Levels of Integration

- Digital circuits are constructed with integrated circuits
- An **integrated circuit** (IC) is a silicon semiconductor crystal (informally a chip) containing the electronic components for the digital gates and storage elements
- **Small-scale integrated** (SSI): Primitive gates, # of gates  $< 10$
- **Medium-scale integrated** (MSI): Elementary digital functions (4-bit addition),  $10 < \text{\# of gates} < 100$
- **Large-scale integrated** (LSI): Small processors, small memories, programmable modules,  $100 < \text{\# of gates} < \text{a few thousand}$
- **Very large-scale integrated** (VLSI): Complex microprocessors and digital signal processing chips, several thousand to tens of millions of gates
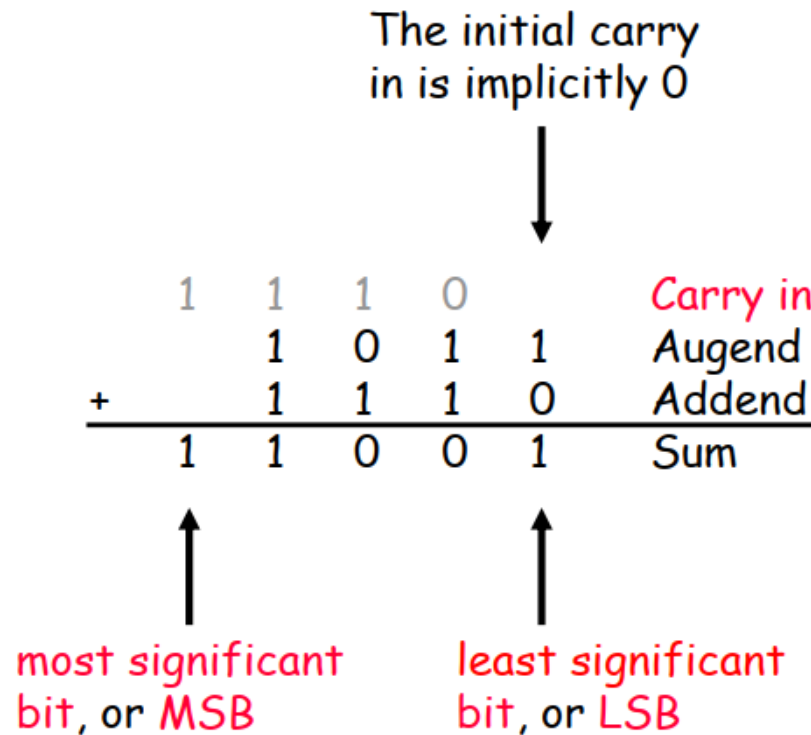
# Arithmetic Functions - Adders



- You can add two binary numbers one column at a time starting from the right, just as you add two decimal numbers
- But remember that it's binary. For example,  $1 + 1 = 10$  and you have to carry!



# Adding Two Bits


- A hardware adder by copying the human addition algorithm
- **Half adder**: Adds two bits and produces a two-bit result: a **sum** (the right bit) and a **carry out** (the left bit)
- Here are truth tables, equations, circuit and block symbol

X	Y	C	S	
0	0	0	0	$0 + 0 = 0$
0	1	0	1	$0 + 1 = 1$
1	0	0	1	$1 + 0 = 1$
1	1	1	0	$1 + 1 = 10$

  

$$C = XY$$

$$S = X'Y + XY'$$
$$= X \oplus Y$$

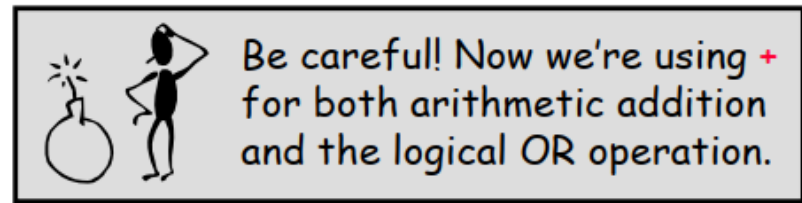

# Adding Tree Bits – Full Adder

- what we really need to do is add three bits: the augend and addend, and the carry in from the right.

$$\begin{array}{r}
 1 \quad 1 \quad 1 \quad 0 \\
 \quad 1 \quad 0 \quad 1 \quad 1 \\
 + \quad 1 \quad 1 \quad 1 \quad 0 \\
 \hline
 1 \quad 1 \quad 0 \quad 0 \quad 1
 \end{array}$$

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$0 + 0 + 0 = 00$$

$$0 + 0 + 1 = 01$$

$$0 + 1 + 0 = 01$$

$$0 + 1 + 1 = 10$$

$$1 + 0 + 0 = 01$$

$$1 + 0 + 1 = 10$$

$$1 + 1 + 0 = 10$$

$$1 + 1 + 1 = 11$$

# Full Adder

- **Full adder**: Three bits of input, two-bit output consisting of a sum and a carry out
- Using Boolean algebra, we get the equations shown here
  - XOR operations simplify the equations a bit
  - We used algebra because you can't easily derive XORs from K-maps

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned} S &= \Sigma m(1,2,4,7) \\ &= X' Y' C_{in} + X' Y C_{in}' + X Y' C_{in}' + X Y C_{in} \\ &= X' (Y' C_{in} + Y C_{in}') + X (Y' C_{in}' + Y C_{in}) \\ &= X' (Y \oplus C_{in}) + X (Y \oplus C_{in})' \\ &= X \oplus Y \oplus C_{in} \end{aligned}$$


$$\begin{aligned} C_{out} &= \Sigma m(3,5,6,7) \\ &= X' Y C_{in} + X Y' C_{in} + X Y C_{in}' + X Y C_{in} \\ &= (X' Y + X Y') C_{in} + X Y (C_{in}' + C_{in}) \\ &= (X \oplus Y) C_{in} + X Y \end{aligned}$$


 
# Full Adder Circuit



These things are called half adders and full adders because you can build a full adder by putting together two half adders!

$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = (X \oplus Y) C_{in} + XY$$



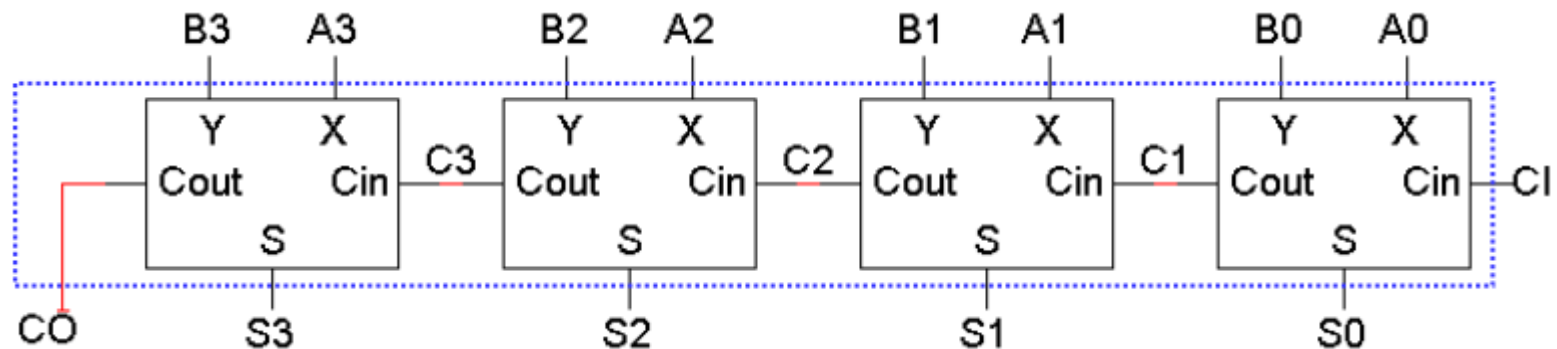 
# A 4-Bit Adder

- Four full adders together make a 4-bit adder
- There are nine total inputs:
  - Two 4-bit numbers, A3 A2 A1 A0 and B3 B2 B1 B0
  - An initial carry in, CI
- The five outputs are:
  - A 4-bit sum, S3 S2 S1 S0
  - A carry out, CO
- Imagine designing a nine-input adder without this hierarchical structure, you'd have a 512-row truth table with five outputs!


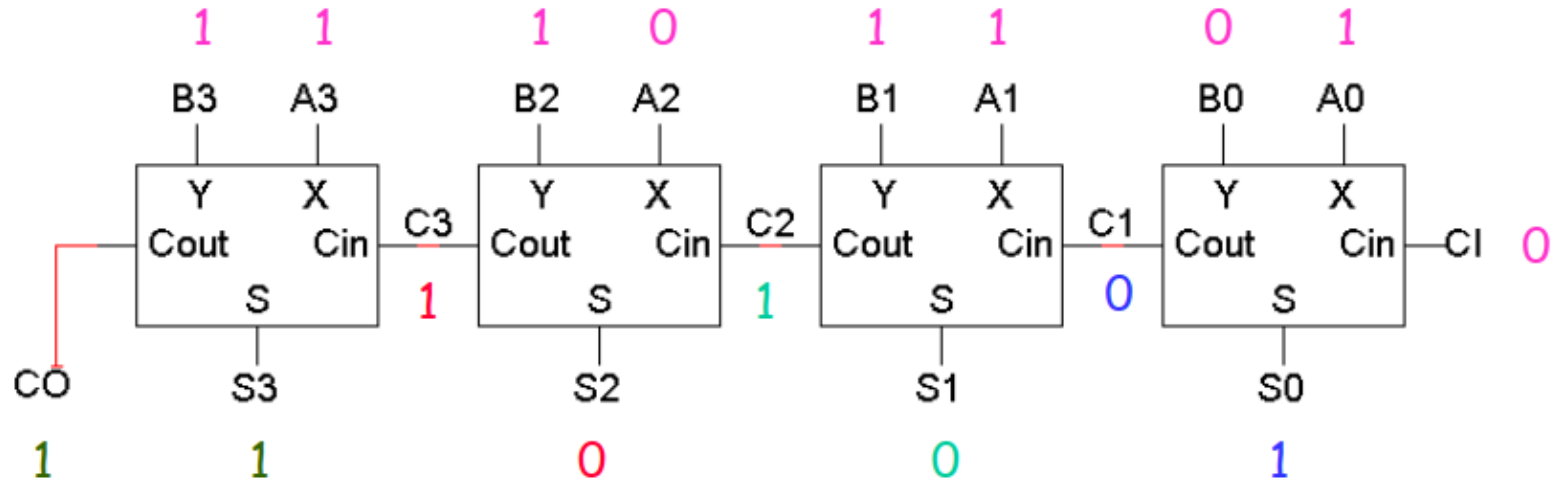
# An example of 4-bit addition

- Let's try our initial example:  $A=1011$  (eleven),  $B=1110$  (fourteen)



1. Fill in all the inputs, including  $CI=0$
2. The circuit produces  $C1$  and  $S0$  ( $1 + 0 + 0 = 01$ )
3. Use  $C1$  to find  $C2$  and  $S1$  ( $1 + 1 + 0 = 10$ )
4. Use  $C2$  to compute  $C3$  and  $S2$  ( $0 + 1 + 1 = 10$ )
5. Use  $C3$  to compute  $CO$  and  $S3$  ( $1 + 1 + 1 = 11$ )

The final answer is 11001 (twenty-five)

In this case, note that the answer (11001) is *five* bits long, while the inputs were each only four bits (1011 and 1110). This is called **overflow**