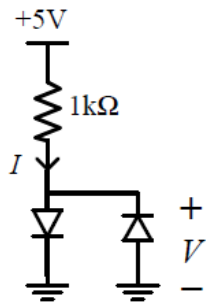


YILDIZ TECHNICAL UNIVERSITY

FACULTY OF ELECTRICAL AND ELECTRONICS ENGINEERING / DEPARTMENT OF BIOMEDICAL ENGINEERING

Name and surname:	Student number:			Signature:	
Course: BME2312 Analog Electronics	Date / Time: 02 May 2021 10:00			Time: 90 minutes	
Exam Type:	Midterm1 x	Midterm2	Make-up for Midterms	Final	Make-up
Title Name-Surname: Assist. Prof. Dr. İsmail CANTÜRK (Instructor)					


1. Assume $0.7V$ constant voltage drop model and determine the values of I and V for below diode circuits. Show your solution steps clearly and explain them. The answers without solution steps will not be graded. Also, state your results in the sections below the circuits.



a)

$$I =$$


$$V =$$

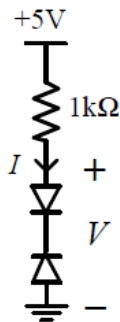

b)

$$I =$$


$$V =$$

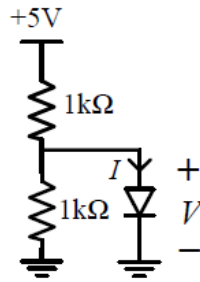

c)

$$I =$$

$$V =$$

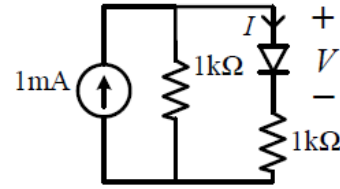

d)

$$I =$$

$$V =$$

2. Consider the below zener diode circuit and find the values of I_{D1} , V_{D1} , I_{D2} , and V_{D2} . Use the constant voltage drop model which is shown in Figure 2. Show your solution steps clearly and explain them. The answers without solution steps will not be graded. Also, state your results in the sections below the circuits. ($I_{Zmin} = 0.1mA$)

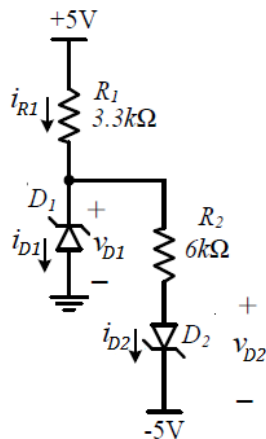


Figure 1

$$I_{D1} =$$

$$V_{D1} =$$

$$I_{D2} =$$

$$V_{D2} =$$


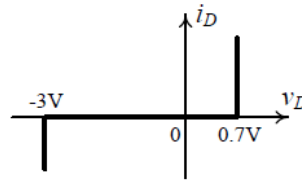


Figure 2

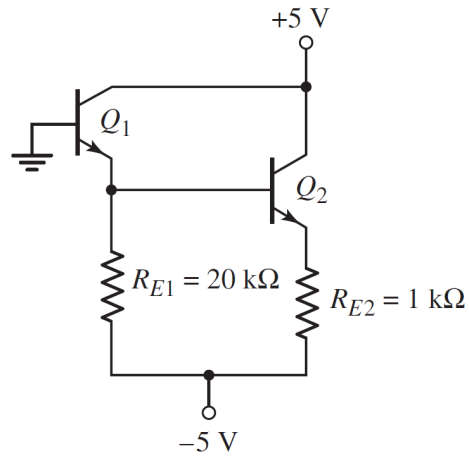3. Consider below BJT circuit and determine base, collector, and emitter currents in Q_1 and Q_2 . Verify your operation mode assumption. Show your solution steps clearly and explain them. The answers without solution steps will not be graded. Also, state your results in the sections below the circuits. ($\beta = 80, V_{BE(on)} = 0.7V$)



$$I_{B1} =$$

$$I_{B2} =$$

$$I_{C1} =$$

$$I_{C2} =$$

$$I_{E1} =$$

$$I_{E2} =$$