

BME2322 – Logic Design

The Instructors:

Dr. Görkem SERBES (C317)

gserbes@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/gserbes/>

Lab Assistants:

Nihat AKKAN


nakkan@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/nakkan>

LECTURE 11

Flip-Flop Conversion

 - Steps:
 - Identify the available and required flip-flop.
 - Write the characteristic table for required flip-flop.
 - Write the excitation table for available flip-flop.
 - Write the Boolean expression for available flip-flop.
 - Draw the circuit.



JK to D flip-flop conversion

1. Available flip-flop is JK and the required flip-flop is D type.
2. Characteristic table of D flip-flop

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Q_n	D	Q_{n+1}	J	K
0	0	0	0	X
0	1	1	1	X
1	0	0	X	1
1	1	1	X	0



3. Excitation table of JK flip-flop

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

4. Boolean Expression

		D	
		0	1
Q_n	0	0	1
	1	X	X


$$J = D$$

		D	
		0	1
Q_n	0	X	X
	1	1	0

$$K = D'$$

JK to D flip-flop conversion cont.

5. Draw the circuit

 

T flip-flop to D flip-flop conversion

1. Available flip-flop is T and the required flip-flop is D type.
2. Characteristic table of D flip-flop

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Q_n	D	Q_{n+1}	T
0	0	0	0
0	1	1	1
1	0	0	1
1	1	1	0




3. Excitation table of T flip-flop

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

4. Boolean Expression

$$T = D \oplus Q_n$$

5. Circuit Diagram

 

SR flip-flop to JK flip-flop conversion

1. Available flip-flop is SR and the required flip-flop is JK type.
2. Characteristic table of JK flip-flop

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



3. Excitation table of SR flip-flop

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0




Q_n	J	K	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	0	0	X
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	1	X	0
1	0	1	0	0	1
1	1	0	1	X	0
1	1	1	0	0	1

SR flip-flop to JK flip-flop conversion cont.

Q_n	J	K	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	0	0	X
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	1	X	0
1	0	1	0	0	1
1	1	0	1	X	0
1	1	1	0	0	1

5. Circuit Diagram

 

4. Boolean Expression

		JK			
		00	01	11	10
Q_n	0	0	0	1	1
	1	X	0	0	X

$$S = \overline{Q_n}J$$


		JK			
		00	01	11	10
Q_n	0	X	X	0	0
	1	0	1	1	0

$$R = Q_nK$$




Preset and Clear inputs

- The normal data inputs to a flip flop (D, S and R, or J and K) are referred to as synchronous inputs because they have an effect on the outputs (Q and not-Q) only in step, or in sync, with the clock signal transitions.
- The 'Preset' and 'Clear' are the direct inputs or overriding inputs or asynchronous inputs.
 - Preset = 0 \rightarrow $Q_n = 1$
 - Clear = 0 \rightarrow $Q_n = 0$
- Whatever be the value of clock and synchronous inputs, 'preset' and 'clear' changes Q_n .
- They can be used in the design of counters.


preset	clear	Q_n
0	0	Not Used
0	1	1
1	0	0
1	1	perform normally

 

Preset and Clear inputs cont

   

Introduction to State Diagrams

 

A sequential circuit

State Table is the table which tells us about the relation between the **present state**, **next state** and the **output**.

Present State		Input x	Next State		Output y
Q _A	Q _B		Q ⁺ _A	Q ⁺ _B	
0	0	1	1	0	1

A random case


State Diagram : 2 flip-flops, so we will have $2^2 = 4$ states.

	Q _A	Q _B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Introduction to State Diagrams cont.

	Q_A	Q_B
S0	0	0
S1	0	1
S2	1	0
S3	1	1


Present State		Input	Next State		Output
Q_A	Q_B	x	Q^+_A	Q^+_B	y
0	0	1	1	0	1

 

State diagram of JK flip-flop

<u>P.S</u> Q_n	<u>Inputs</u> J K		<u>N.S</u> Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 - We have two possible states;
 - $S0 = 0$
 - $S1 = 1$



State diagram of JK flip-flop

State equation of JK flip-flop

<u>P.S</u> Q_n	<u>Inputs</u> J K		<u>N.S</u> Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		JK			
		00	01	11	10
Q_n	0	0	0	1	1
	1	1	0	0	1

$$Q_{n+1} = Q_n \cdot K' + (Q_n)' \cdot J$$

State equation

- State Equation \rightarrow left hand side = right hand side

\downarrow
 Next State


\downarrow
 Combination of the present
state and input

Sequential Circuit Analysis


- The output of a sequential circuit can be expressed in two different ways:

- Moore model: $\text{Outputs} = f(\text{present state})$
- Mealy model: $\text{Outputs} = f(\text{present state, inputs})$

Moore machine:

 


Example 1

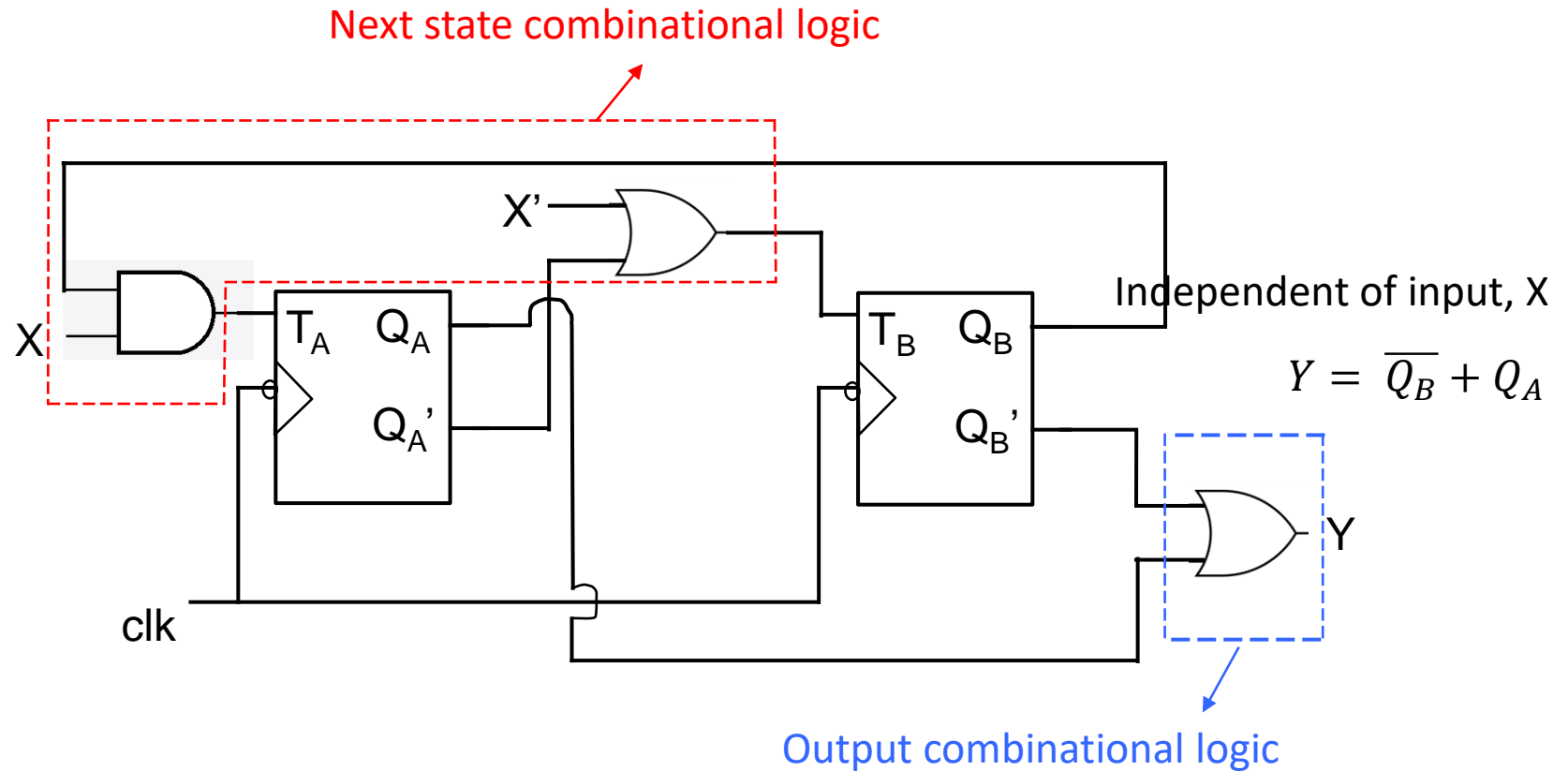


The circuit is a Moore Machine

Example 2 (Moore)

 

- Two inputs: X and Y; One output: Z
- One state: A
- Note that $Z = A$, just a function of the current state

Example 2 (Moore) cont.

 

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


(b) State table

Present State A	Next State				Output Z
	Inputs XY				
	00	01	10	11	
0	0	1	1	0	0
1	1	0	0	1	1

Example 2 (Moore) cont.


Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b) State table

 


Mealy Machine

 - The output is the function of present state as well as the input.




Comparision with Example 1

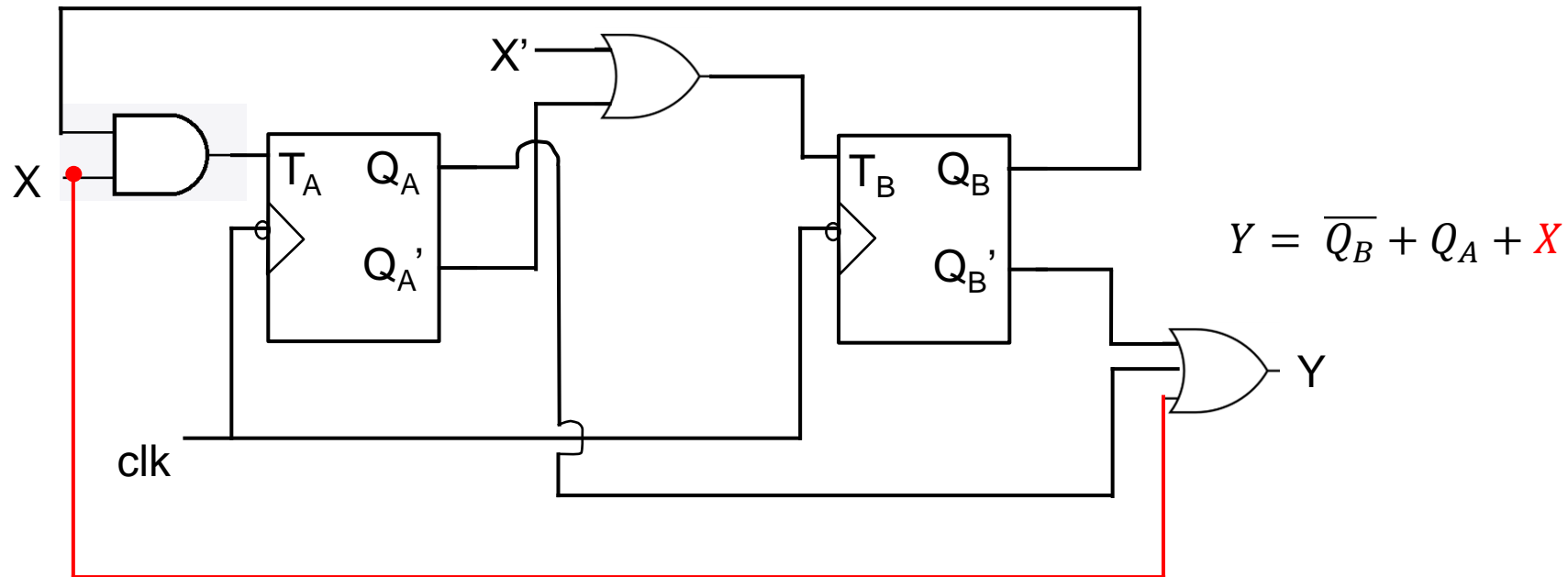

The circuit is a Mealy Machine

Analysis of clocked circuits with D ff

 

Step 1: Write Input and Output Equations


$$D_A = X \cdot Q_A + Q_B$$

$$D_B = \overline{Q_A} \cdot Q_B$$

$$Y = X \cdot Q_A + \bar{X} \cdot \overline{Q_B}$$

CLK	D	Q_{n+1}
0	X	Q_n
1	0	0
1	1	1

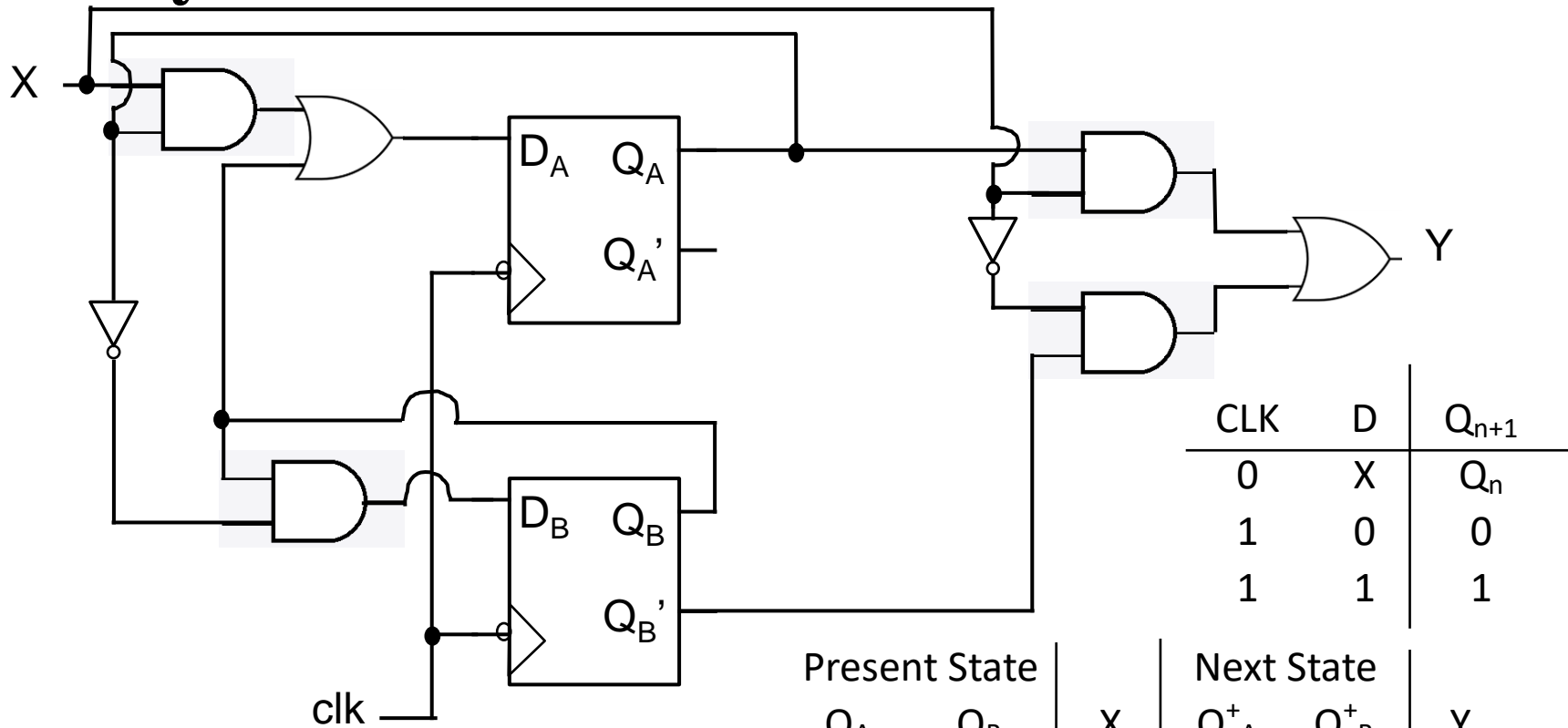Analysis of clocked circuits with D ff cont.



Step 2: Find state table

Present State			Next State		
Q_A	Q_B	X	Q_A^+	Q_B^+	Y
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	0	1

$$D_A = X \cdot Q_A + Q_B$$

$$D_B = \overline{Q_A} \cdot Q_B$$

$$Y = X \cdot Q_A + \overline{X} \cdot \overline{Q_B}$$

Analysis of clocked circuits with D ff cont.


Present State

Next State


Q_A	Q_B	X	Q_A^+	Q_B^+	Y
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	0	1

	Q_A	Q_B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Step 3: Find state diagram

 

Analysis of clocked circuits with JK ff

 

Step 1: Input Equations, No Output Equation

$$J_A = Q_B \quad K_A = \bar{X}.J_A$$

$$J_B = \bar{X} \quad K_B = X \oplus Q_A = \bar{X} \cdot Q_A + X \cdot \overline{Q_A}$$

Analysis of clocked circuits with JK ff cont.


$$J_A = Q_B \quad K_A = \bar{X} \cdot J_A$$

$$J_B = \bar{X} \quad K_B = X \oplus Q_A = \bar{X} \cdot Q_A + X \cdot \bar{Q}_A$$

CLK	J	K	Q_{n+1}
0	X	X	Q_n
1	0	0	Q_n
1	0	1	0
1	1	0	1
1	1	1	$(Q_n)'$

Step 2: Find the state table

Present State							Next State	
Q_A	Q_B	X	J_A	K_A	J_B	K_B	Q_A^+	Q_B^+
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

 


Analysis of clocked circuits with JK ff cont.


Present State							Next State	
Q_A	Q_B	X	J_A	K_A	J_B	K_B	Q_A^+	Q_B^+
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

	Q_A	Q_B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Step 3: Find state diagram

 

Analysis of clocked circuits with T ff

 

Step 1: Input Output Combinational Equation

$$T_A = X$$

$$T_B = X \cdot Q_A$$


$$Y = Q_A \cdot Q_B$$

Analysis of clocked circuits with T ff cont.

$$T_A = X$$

$$T_B = X \cdot Q_A$$

$$Y = Q_A \cdot Q_B$$

 

Step 2: Find the state table


Present State		X	T_A	T_B	Next State		Y
Q_A	Q_B				Q_A^+	Q_B^+	
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	1	0	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	1

CLK	T	Q_{n+1}
0	X	Q_n
1	0	Q_n
1	1	$(Q_n)'$

Analysis of clocked circuits with T ff cont.

Present State						Next State		
Q_A	Q_B	X	T_A	T_B		Q^+_A	Q^+_B	Y
0	0	0	0	0		0	0	0
0	0	1	1	0		1	0	0
<hr/>								
0	1	0	0	0		0	1	0
0	1	1	1	0		1	1	0
<hr/>								
1	0	0	0	0		1	0	0
1	0	1	1	1		0	1	0
<hr/>								
1	1	0	0	0		1	1	1
1	1	1	1	1		0	0	1

Step 3: Find state diagram

 

Moore Machine