

BME2322 – Logic Design

The Instructors:

Dr. Görkem SERBES (C317)

gserbes@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/gserbes/>

Lab Assistants:

Nihat AKKAN


nakkan@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/nakkan>

LECTURE 8

Multiplexers

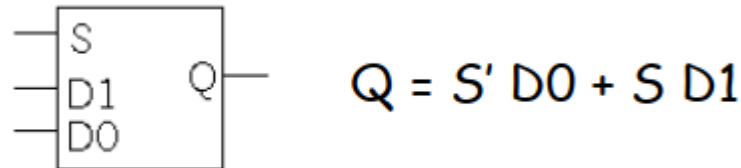
- A 2^n -to-1 multiplexer sends one of 2^n input lines to a single output line
 - A multiplexer has two sets of inputs:
 - 2^n data input lines
 - n select lines, to pick one of the 2^n data inputs
 - The mux output is a single bit, which is one of the 2^n data inputs
- The simplest example is a 2-to-1 mux:



- The select bit S controls which of the data bits $D0$ - $D1$ is chosen:
 - If $S=0$, then $D0$ is the output ($Q=D0$).
 - If $S=1$, then $D1$ is the output ($Q=D1$).

Truth table representation

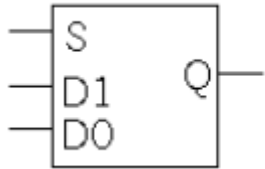- Here is a full truth table for this 2-to-1 mux, based on the equation:




$$Q = S' D0 + S D1$$

S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Here is another kind of abbreviated truth table
 - Input variables appear in the output column
 - This table implies that when $S=0$, the output $Q=D0$, and when $S=1$ the output $Q=D1$
 - This is a close match to the equation

S	Q
0	D0
1	D1

2-to-1 Mux

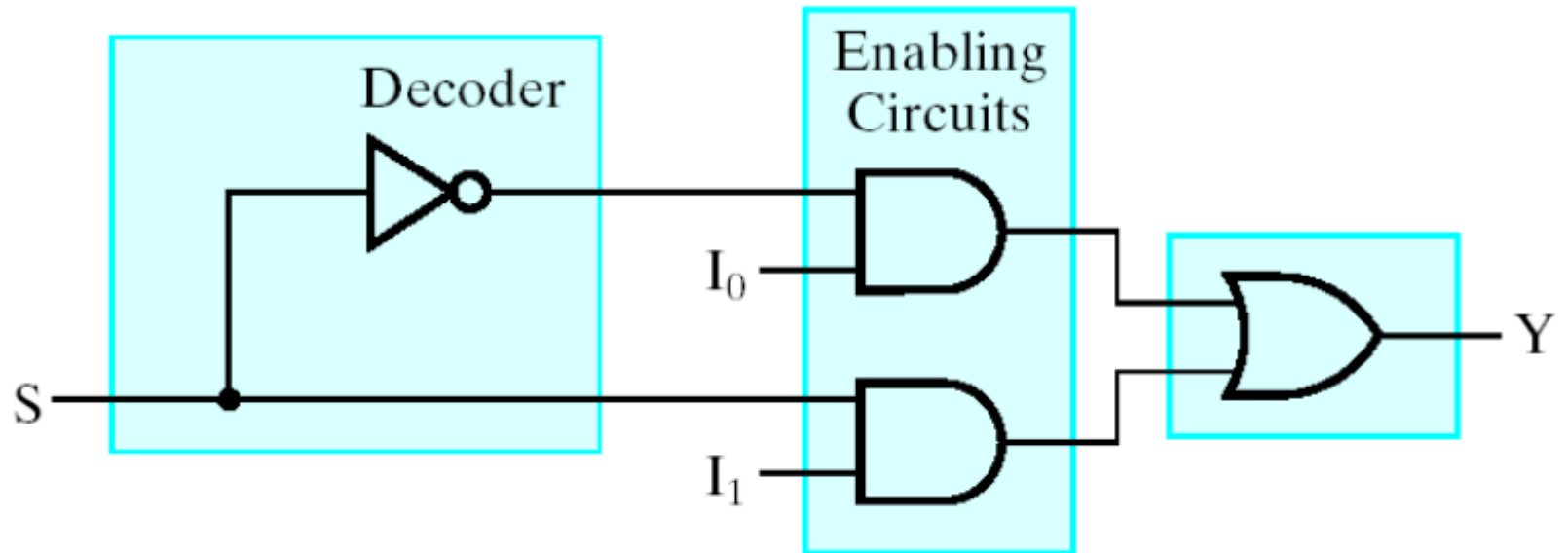


4-to-1 Mux

Condensed Truth Table for 4-to-1-Line Multiplexer


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Y = (S_1'S_0')I_0 + (S_1'S_0)I_1 + (S_1S_0')I_2 + (S_1S_0)I_3$$


Decoder



4-to-1 Mux

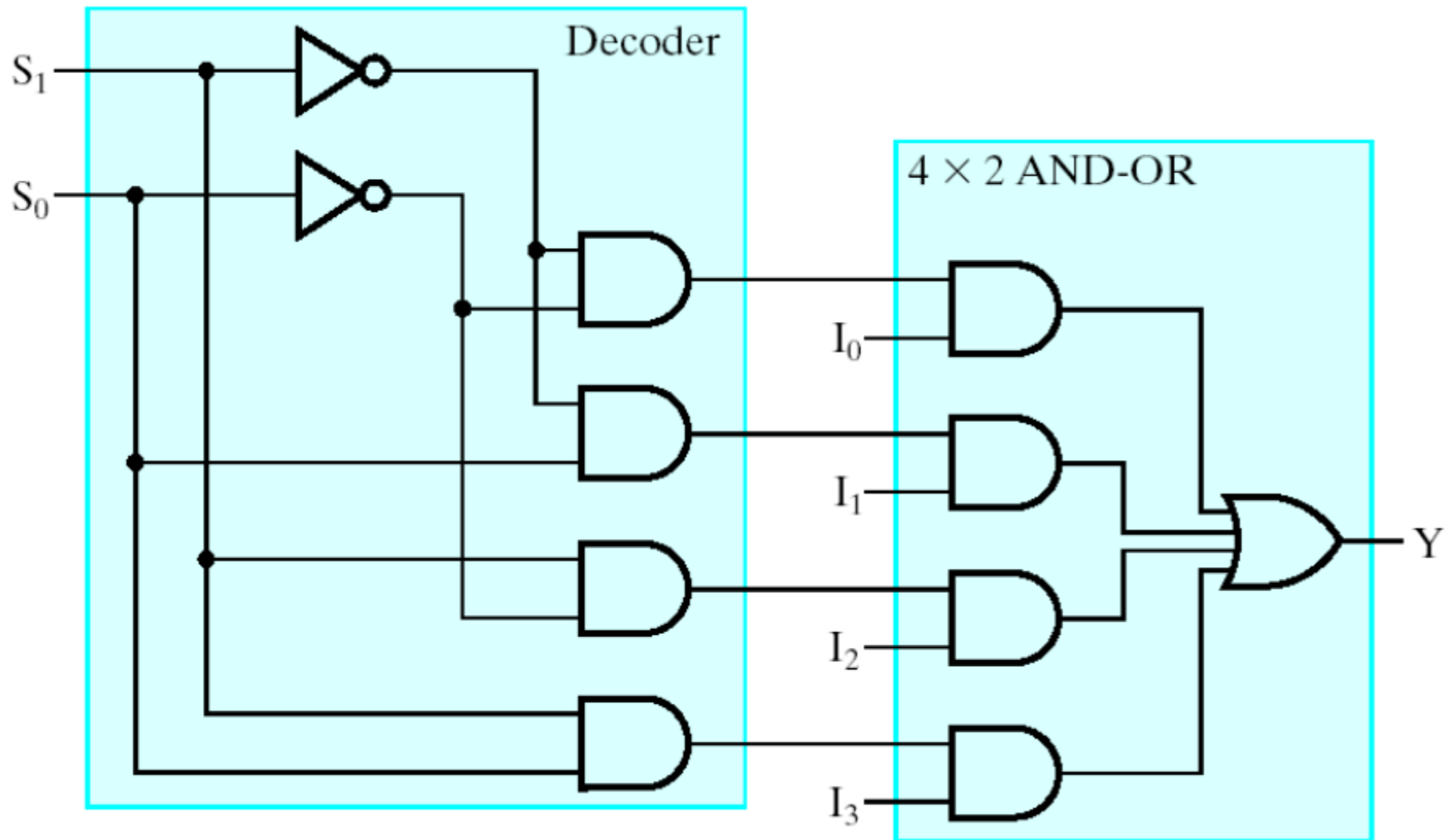

4-to-1 Mux with Enable Input

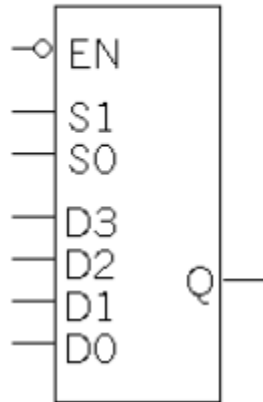


EN	S1	S0	Q
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	x	x	1

$$Q = \overline{EN} \overline{S1} \overline{S0} D0 + \overline{EN} \overline{S1} S0 D1 + \overline{EN} S1 \overline{S0} D2 + \overline{EN} S1 S0 D3 + EN$$

Implementing functions with multiplexers

- Muxes can be used to implement arbitrary functions
- One way to implement a function of n variables is to use an 2^n -to-1 mux:
 - For each minterm m_i of the function, connect 1 to mux data input D_i . Each data input corresponds to one row of the truth table
 - Connect the function's input variables to the mux select inputs. These are used to indicate a particular input combination
- For example, let's look at $f(x,y,z) = \sum m(1,2,6,7)$.


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

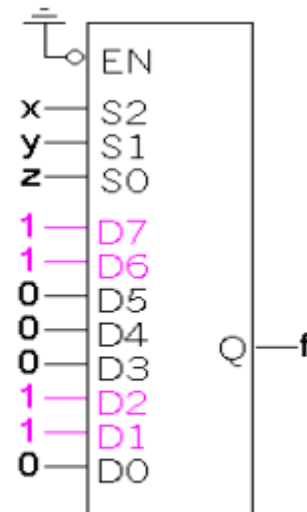

A more efficient way

- We can actually implement $f(x,y,z) = \sum m(1,2,6,7)$ with just a 4-to-1 mux, instead of an 8-to-1
- Step 1: Find the truth table for the function, and group the rows into pairs. Within each pair of rows, x and y are the same, so f is a function of z only.
 - When $xy=00$, $f=z$
 - When $xy=01$, $f=z'$
 - When $xy=10$, $f=0$
 - When $xy=11$, $f=1$
- Step 2: Connect the first two input variables of the truth table (here, x and y) to the select bits S1 S0 of the 4-to-1 mux.
- Step 3: Connect the equations above for f(z) to the data inputs D0-D3.

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

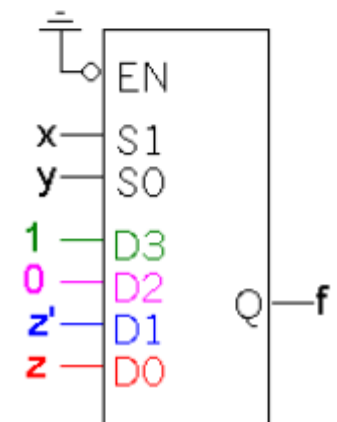


Example 1

- Implement a 4×1 mux by using 2×1 muxes

Example 2

- Implement a 8×1 mux by using 2×1 muxes

Example 2 Cont.

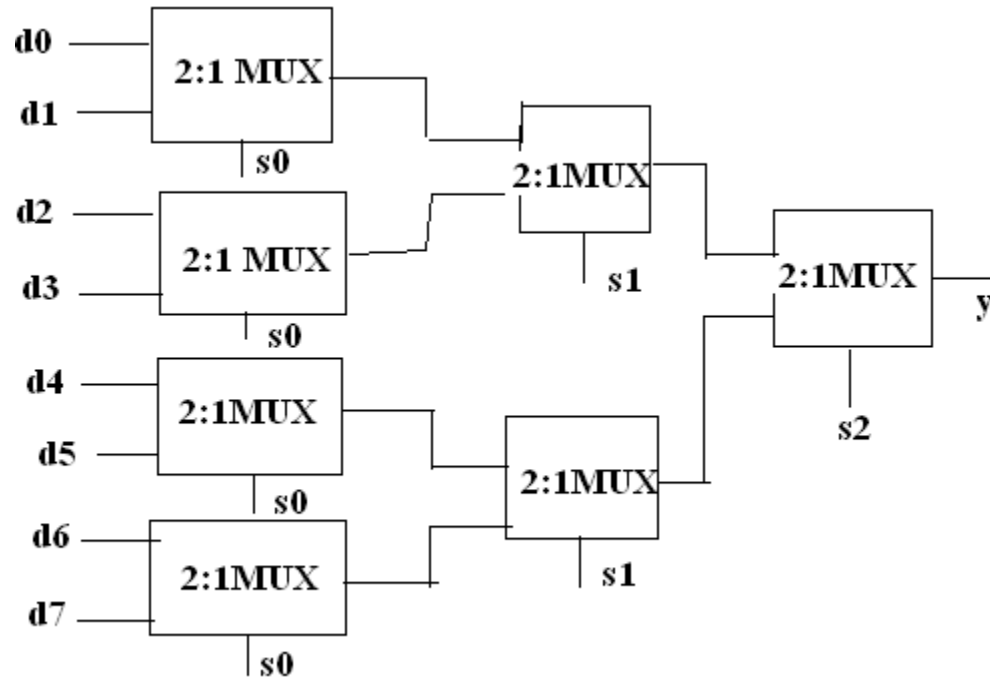

Example 3

- Implement a 8×1 mux by using 4×1 muxes

Example 4

- Implement $F(A,B,C,D) = \sum m(1,4,5,7,9,12,13)$ using a 4×1 mux

Summary of Multiplexers

- A 2^n -to-1 multiplexer routes one of 2^n input lines to a single output line
- Just like decoders,
 - Muxes are common enough to be supplied as stand-alone devices for use in modular designs.
 - Muxes can implement arbitrary functions
- We saw some variations of the standard multiplexer:
 - Smaller muxes can be combined to produce larger ones
 - We can add active-low or active-high enable inputs
- As always, we use truth tables and Boolean algebra to analyze things