

BME2322 – Logic Design

The Instructors:

Dr. Görkem SERBES (C317)

gserbes@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/gserbes/>

Lab Assistants:

Nihat AKKAN


nakkan@yildiz.edu.tr

<https://avesis.yildiz.edu.tr/nakkan>

LECTURE 3


Inside the Digital Gates

Inside the Digital Gate

 

The Digital Abstraction

 - Discretize value: 0, 1
- Static discipline -- digital devices meet voltage thresholds




Specifies how gates must be designed

Combinational Elements


Combinational gate abstraction

 - outputs function of input alone
- satisfies static discipline



A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


A digital circuit

 

3 gates here

If we use combination of simple gates

How to build a digital gate

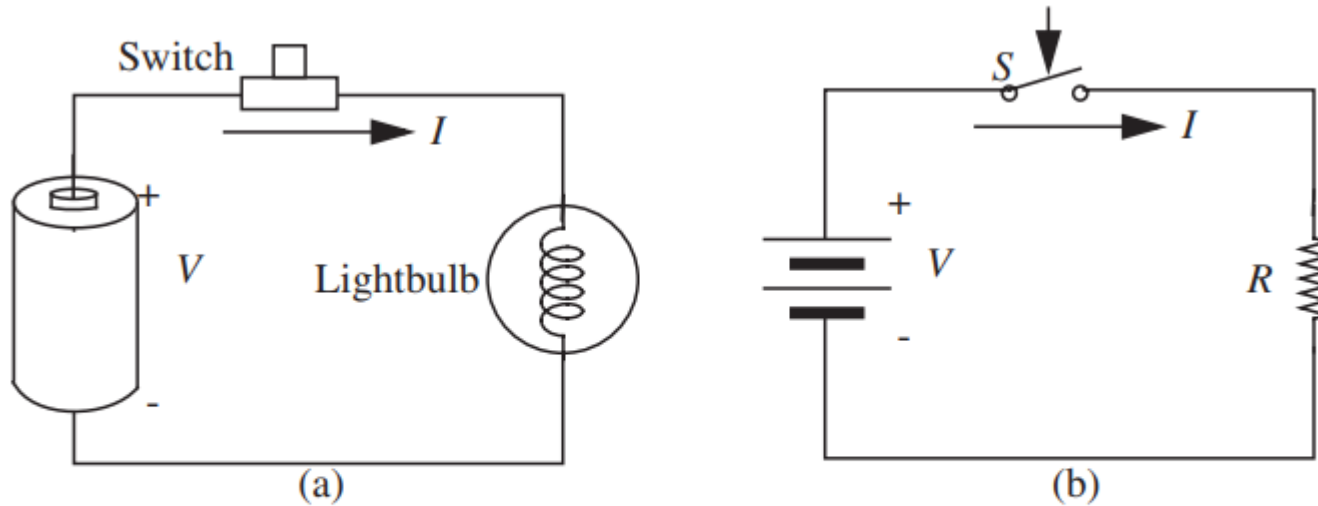


(a) The lightbulb circuit with a switch; (b) the lumped circuit representation.

The switch is normally off and behaves like an open circuit. When pressure is applied to the switch, it closes and behaves like a wire and conducts current.



Accordingly, the switch can be modeled as the three-terminal device

How to build a digital gate

 When the control terminal has a TRUE or a logical 1 signal on it, the input is connected to the output through a short circuit.



  Otherwise, there is an open circuit between the input and the output.




v - i Characteristics of the Switch

The v - i characteristics of a switch can also be expressed in algebraic form as:

for Control = "0," $i = 0$

and



for Control = "1," $v = 0$.

 


v - i characteristics of a switch. v is the voltage across the input and the output terminals of the switch and i is the current through the same pair of terminals.

Logic Functions using Switches

  
(a) The lightbulb circuit with switch in an *AND* configuration; (b) the lightbulb circuit with switches in an *OR* configuration.



Using Three Terminal Switch Device

 

Behavior of this Basic Circuit

 


NOT Gate



egot.

C	z
0	1
1	0

NAND Gate

 


c_1	c_2	z
0	0	1
0	1	1
1	0	1
1	1	0

Truth table for



NOR Gate

 


C_1	C_2	Z
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table for ?



An Example

We can also build compound gates

 


Now let's get back to reality... we need a physical switch

Example 1


In the figure shown there are three circuits. The first two, labeled "a" and "b", are an inverter and a NOR gate, respectively. Circuit "c" is a bit more complex.

Z = ?

 

The MOSFET Device

 
Metal-Oxide Semiconductor
Field-Effect Transistor



3 terminal lumped element
behaves like a switch

Port representation
of a MOSFET.


Similar to switch

 


G : control terminal

D, S : behave in a symmetric
manner (for our needs)


The MOSFET Device (S model)

 

$v_{GS} < V_T$

 


$v_{GS} \geq V_T$

 


$V_T \sim 1V$
for example

MOSFET Device on Scope

 





A MOSFET Inverter

 


Note the power of abstraction:

The abstract inverter gate representation hides internal details such as power supply connections, R_L , GND , etc. When we build digital circuits, the \uparrow and \perp are common across all gates!

Input – Output Voltage Relation

    


Called voltage transfer characteristic

 

An Inverter Design (Consider Static Discipline)

 Question: The T1000 model laptop needs gates that satisfy a static discipline with voltage thresholds given below. Does our inverter qualify?




$$V_{OL} = 0.5V \quad V_{IL} = 0.9V$$


$$V_{OH} = 4.5V \quad V_{IH} = 4.1V$$

1:

sender

 

0:

 


1

receiver


0

An Inverter Design (Consider Static Discipline)

 
Does our inverter satisfy the voltage thresholds for this static discipline?


 
$$\begin{array}{ll} V_{OL} = 0.5V & V_{IL} = 0.9V \\ V_{OH} = 4.5V & V_{IH} = 4.1V \end{array}$$





Our Inverter

 

An Inverter Design (Consider Static Discipline)

  Does our inverter satisfy the static discipline for these different thresholds?





$V_{OL} = 0.2V$	$V_{IL} = 0.5V$
$V_{OH} = 5.1V$	$V_{IH} = 4.5V$

$V_{OL} = 0.2V$	$V_{IL} = 0.5V$
$V_{OH} = 5.1V$	$V_{IH} = 4.5V$

An Inverter Design (Consider Static Discipline)

How about these thresholds?

  


$V_{OL} = 0.5V$	$V_{IL} = 1.5V$
$V_{OH} = 4.5V$	$V_{IH} = 3.5V$

$$V_{OL} = 0.5V \quad V_{IL} = 1.5V$$

$$V_{OH} = 4.5V \quad V_{IH} = 3.5V$$

Example 2

 

The graph shows the input/output behavior of the inverter, given the S-model (perfect switch model) of the MOSFET. The inverter shown must meet the static discipline: $0 \leq V_{OL} < V_{IL} < V_{IH} < V_{OH} \leq V_S$




The required discipline is: $V_{OL} = 0.32V$, $V_{IL} = 0.5760000000000001V$, $V_{IH} = 2.6240000000000006V$, $V_{OH} = 2.88V$, and $V_S = 3.2V$.

For what values of the MOS threshold V_T can the design satisfy the static discipline?

What is the minimum possible value of V_T (in Volts)?





What is the maximum possible value of V_T (in Volts)?

   Switch-Resistor (SR) Model – More Accurate




e.g. $R_{ON} = 5k\Omega$


SR Model of MOSFET

    

Using SR Model - Inverter

 

 when the input v_{IN} is high (and above the threshold V_T), the MOSFET is on and displays a resistance R_{ON} between its D and S terminals, thereby pulling the output voltage lower




when the input is low, the MOSFET is off, and the output is raised to a high value

$$v_{OUT} = V_S \frac{R_{ON}}{R_{ON} + R_L}.$$

Using SR Model - Inverter

The resulting inverter transfer characteristics, assuming $V_S = 5\text{ V}$, $V_T = 1\text{ V}$, $R_{ON} = 1\text{ k}\Omega$, and $R_L = 14\text{ k}\Omega$, are shown in Figure. Notice that the lowest output voltage of the inverter is no longer 0 V , rather it is
 
$$V_S \frac{R_{ON}}{R_{ON} + R_L} = 0.33\text{ V}.$$





Inverter transfer characteristics using the SR model.



Static Discipline Criteria

When the R_L/R_{ON} ratio is 10.

  Does our inverter satisfy the voltage thresholds for this static discipline?



$V_{OL} = 0.5V$	$V_{IL} = 0.9V$
$V_{OH} = 4.5V$	$V_{IH} = 4.1V$

  


Example 3

For this problem, consider the convention that a logical one corresponds to a high voltage level and a logical zero corresponds to a low voltage level. Thus, when the voltage v_A associated with the Boolean variable A is high, A is one. When v_A is low, A is zero. The same holds for v_B and B, and v_C and C. Assume also the following:

- The high voltage level is much greater than the threshold voltage,
- The "on" resistance of the MOSFET is 50.0Ω ,
- The "off" resistance of the MOSFET is $10\text{M}\Omega$.

 For each of the following diagrams we provide a corresponding truth table. You will provide the value of the output voltage v_C for each row of the table. We will refer to a row by an index placed next to the logical value of C in the table.



A	C
0	1 i
1	0 j


What is the value of v_C (in Volts) at entry i?



What is the value of v_C (in Volts) at entry j?



Example 3 Cont.

 

A	B	C
0	0	1 k
0	1	1 l
1	0	1 m
1	1	0 n

What is the value of v_C (in Volts) at entry k?



What is the value of v_C (in Volts) at entry l?




What is the value of v_C (in Volts) at entry m?



What is the value of v_C (in Volts) at entry n?



Example 3 Cont.

 

A	B	C
0	0	1 o
0	1	0 p
1	0	0 q
1	1	0 r

What is the value of v_C (in Volts) at entry o?

2.9988



What is the value of v_C (in Volts) at entry p?

0.073167162577



What is the value of v_C (in Volts) at entry q?

0.073167162577



What is the value of v_C (in Volts) at entry r?


0.037037



Static Power – NAND Gate Example

In this case, the output voltage when both inputs are high is given by
 
$$v_{\text{OUT}} = V_S \frac{2R_{\text{ON}}}{2R_{\text{ON}} + R_L}.$$



SR circuit model for NAND gate.

Demo – Analog and Digital Elements

