

# BME2322 – Logic Design

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN

[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>


# LECTURE 9

# Sequential Circuits

- We will focus on **sequential circuits**, where we add memory to the hardware that we've already seen (combinational circuits)
- Our plan will be very similar to before:
  - We first show how primitive memory units are built
  - Then we talk about analysis and design of sequential circuits
  - We also see common sequential devices like registers and counters
- We will start with latches

 
# Let's remember combinational circuits

- So far, we've just worked with **combinational circuits**, where applying the same inputs always produces the same outputs
- This corresponds to a mathematical function, where every input has a single, unique output


 
# Sequential circuits

- In contrast, the outputs of a **sequential circuit** depend on not only the inputs, but also the **state**, or the current contents of some memory.
- In sequential circuits, the present output depends on the present input as well as past output/outputs.
- This makes things more difficult to understand, since the same inputs can yield different outputs, depending on what's stored in memory.
- The memory contents can also change as the circuit runs.
- We'll some need new techniques for analyzing and designing sequential circuits.





# A memory element

- A memory element should have at least three properties
  1. It should be able to hold a value.
  2. You should be able to read the value that was saved.
  3. You should be able to change the value that's saved.
- We'll start with the simplest case, a one-bit memory
  1. It should be able to hold a single bit, 0 or 1.
  2. You should be able to read the bit that was saved.
  3. You should be able to change the value.
- Since there's only a single bit, there are only two choices:
  - **Set** the bit to 1
  - **Reset**, or **clear**, the bit to 0
  
# How can we store a bit?


- How can a circuit “remember” anything, when it’s just a bunch of gates that produce outputs according to the inputs?
- The basic idea is to make a loop, so the circuit outputs are also inputs
- Here is one initial attempt, shown with two equivalent layouts:



- Does this satisfy the properties of memory?
  - These circuits “remember”  $Q$ , because its value never changes (Similarly,  $Q'$  never changes either.)
  - We can also “read”  $Q$ , by attaching a probe or another circuit
  - But we can’t change  $Q$ ! There are no external inputs here, so we can’t control whether  $Q=1$  or  $Q=0$ .
 
# SR latch circuit

- Let's use NOR gates instead of inverters. The **SR latch** below has two inputs S and R, which will let us control the outputs Q and Q'



- Here Q and Q' feed back into the circuit. They're not only outputs, they're also inputs!
- To figure out how Q and Q' change, we have to look at not only the inputs S and R, but also the current values of Q and Q':

$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$
$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$

- Let's see how different input values for S and R affect this thing




# Storing a value: SR = 00

- What if  $S = 0$  and  $R = 0$ ?
- The equations on the right reduce to:

$$Q_{\text{next}} = (0 + Q'_{\text{current}})' = Q_{\text{current}}$$
$$Q'_{\text{next}} = (0 + Q_{\text{current}})' = Q'_{\text{current}}$$

 - So when  $SR = 00$ , then  $Q_{\text{next}} = Q_{\text{current}}$ .  
Whatever value  $Q$  has, it keeps
- This is exactly what we need, to **store** values in the latch.
- It works as a memory element.



$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$
$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$

TRUTH TABLE

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

# Setting the latch: SR = 10


- What if  $S = 1$  and  $R = 0$ ?
- Since  $S = 1$ ,  $Q'_{\text{next}}$  is 0, regardless of  $Q_{\text{current}}$ :

$$Q'_{\text{next}} = (1 + Q_{\text{current}})' = 0$$

- Then, this new value of  $Q'$  goes into the top NOR gate, along with  $R = 0$ .

$$Q_{\text{next}} = (0 + 0)' = 1$$

 - So, when  $SR = 10$ , then  $Q'_{\text{next}} = 0$  and  $Q_{\text{next}} = 1$
- This is how you **set** the latch to 1. The S input stands for “set”.
- Notice that it can take up to two steps (two gate delays) from the time S becomes 1 to the time  $Q_{\text{next}}$  becomes 1
- But once  $Q_{\text{next}}$  becomes 1, the outputs will stop changing. This is the **stable state**.



$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$

$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$

TRUTH TABLE

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

# Latch delay


- Timing diagrams are especially useful in understanding how sequential circuits work.
- Here is a diagram which shows an example of how our latch outputs change with inputs SR=10.

0. Suppose that initially,  $Q = 0$  and  $Q' = 1$ .


1. Since  $S=1$ ,  $Q'$  will change from 1 to 0 after one NOR-gate delay (marked by vertical lines in the diagram for clarity).

2. This change in  $Q'$ , along with  $R=0$ , causes  $Q$  to become 1 after another gate delay.

 3. The latch then stabilizes until  $S$  or  $R$  change again.


 
$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$
$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$



# Resetting the latch: $SR = 01$


- What if  $S = 0$  and  $R = 1$ ?
- Since  $R = 1$ ,  $Q_{\text{next}}$  is 0, regardless of  $Q_{\text{current}}$ :

$$Q_{\text{next}} = (1 + Q'_{\text{current}})' = 0$$

- Then, this new value of  $Q$  goes into the bottom NOR gate, where  $S = 0$

$$Q'_{\text{next}} = (0 + 0)' = 1$$

 - So, when  $SR = 01$ , then  $Q_{\text{next}} = 0$  and  $Q'_{\text{next}} = 1$
- This is how you reset, or clear, the latch to 0. The  $R$  input stands for “reset”
- Again, it can take two gate delays before a change in  $R$  propagates to the output  $Q'_{\text{next}}$



$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$
$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$

TRUTH TABLE

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

# Forbidden case $SR = 11$ ?

- Both  $Q_{next}$  and  $Q'_{next}$  will become 0
- This contradicts the assumption that  $Q$  and  $Q'$  are always complements
- Another problem is what happens if we then make  $S = 0$  and  $R = 0$  together.

$$Q_{next} = (0 + 0)' = 1$$

$$Q'_{next} = (0 + 0)' = 1$$



- But these new values go back into the NOR gates, and in the next step we get:

$$Q_{next} = (0 + 1)' = 0$$

$$Q'_{next} = (0 + 1)' = 0$$

- The circuit enters an infinite loop, where  $Q$  and  $Q'$  cycle between 0 and 1 forever
- This is the worst case, therefore  $SR=11$  combination is forbidden.
  
$$Q_{next} = (R + Q'_{current})'$$
$$Q'_{next} = (S + Q_{current})'$$



# SR latches work as memory elements!

- This little table shows that our latch provides everything we need in a memory: we can set it, reset it, and remember the current value.
- The output Q represents the data stored in the latch. It is sometimes called the **state** of the latch.
- We can expand the table above into a **state table**, which explicitly shows that the next values of Q and Q' depend on their current values, as well as on the inputs S and R.

S	R	Q
0	0	No change
0	1	0 (reset)
1	0	1 (set)

Inputs		Current		Next	
S	R	Q	Q'	Q	Q'
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0

# SR latches are sequential!


- Notice that for inputs  $SR = 00$ , the next value of  $Q$  could be either 0 or 1, depending on the current value of  $Q$ .
- So, the same inputs can yield different outputs, depending on whether the latch was previously set or reset.
- This is very different from the combinational circuits that we've seen so far, where the same inputs always yield the same outputs.

S	R	Q
0	0	No change
0	1	0 (reset)
1	0	1 (set)

Inputs		Current		Next	
S	R	Q	Q'	Q	Q'
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
 
# S'R' latch using NAND gates

- There are several varieties of latches
- You can use NAND instead of NOR gates to get a **S'R' latch**




S'	R'	Q
1	1	No change
1	0	0 (reset)
0	1	1 (set)
0	0	Avoid!

- This is just like an SR latch, but with inverted inputs, as you can see from the table
- You can derive this table by writing equations for the outputs in terms of the inputs and the current state, just as we did for the SR latch


 
# An SR latch with a control input


- Here is an SR latch with a control input C



- Notice the hierarchical design!
  - The dotted blue box is the S'R' latch from the previous slide
  - The additional NAND gates are simply used to generate the correct inputs for the S'R' latch
- The control input acts just like **an enable**
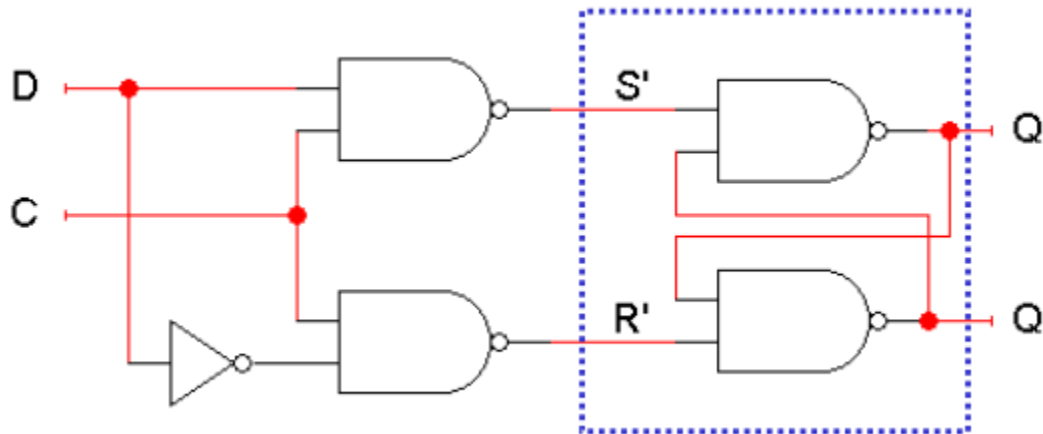
# D latch

- Finally, a D latch is based on an S'R' latch (latch with NAND gates). The additional gates generate the S' and R' signals, based on inputs D ("data") and C ("control")
  - When  $C = 0$ , S' and R' are both 1, so the state Q does not change
  - When  $C = 1$ , the latch output Q will equal the input D
- No more messing with one input for set and another input for reset!




C	D	Q
0	x	No change
1	0	0
1	1	1

- Also, this latch has no "bad" input combinations to avoid. Any of the four possible assignments to C and D are valid.
 
# Sequential circuits and state diagrams

- To describe combinational circuits, we used Boolean expressions and truth tables. With sequential circuits, we can still use expression and tables, but we can also use another form called a **state diagram**
- We draw one node for each state that the circuit can be in. Latches have only two states:  $Q=0$  and  $Q=1$
- Arrows between nodes are labeled with “input/output” and indicate how the circuit changes states and what its outputs are. In this case the state and the output are the same
- Here’s a state diagram for a D latch with inputs D and C



C	D	Q
0	x	No change
1	0	0
1	1	1

# Summary

- A sequential circuit has memory. It may respond differently to the same inputs, depending on its current state
- Memories can be created by making circuits with feedback
  - Latches are the simplest memory units, storing individual bits
  - It's difficult to control the timing of latches in a larger circuit
- Next, we'll improve upon latches with **flip-flops**, which change state only at well-defined times. We will then use flip-flops to build all of our sequential circuits