

# BME2322 – Logic Design

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN


[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>

# LECTURE 7

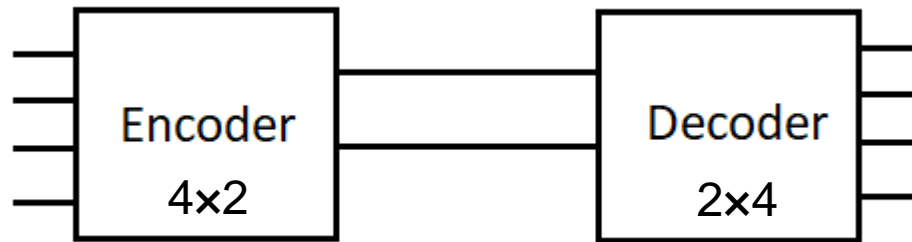
# What is a decoder and encoder?

- A **decoder** is a combinational circuit that converts binary information from 'n' input lines to a maximum of  $2^n$  unique output lines.
- They are called as n-to-m line decoders, where  $m \leq 2^n$



- An **encoder** is a combinational circuit that performs the inverse operation of a decoder. An encoder has  $2^n$  (or. fewer) input lines and 'n' output lines. The output lines generate a binary code corresponding to the input value.

# What is a decoder?

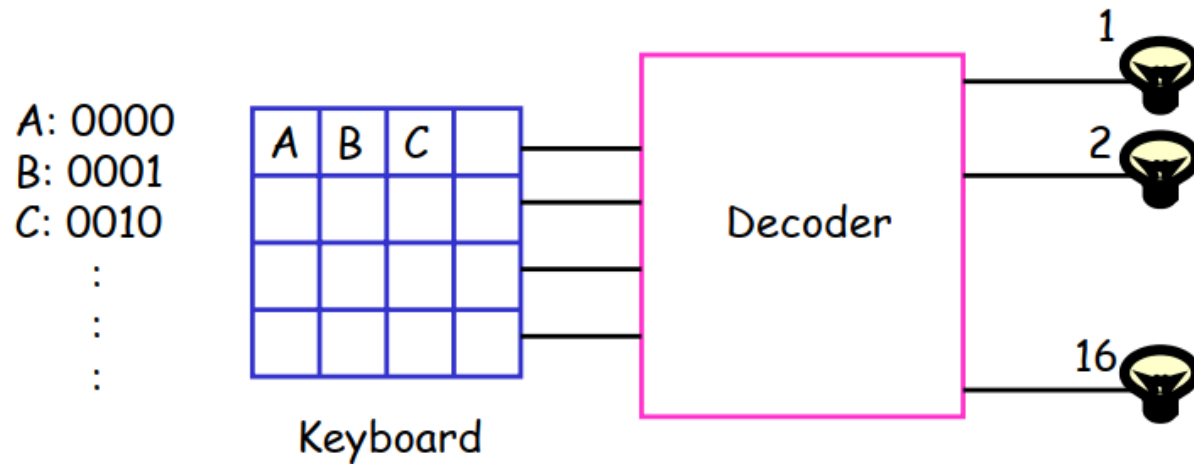


- $n \leq m \leq 2^n$
- Detect which of the  $2^n$  combinations is represented at the inputs
- Produces m number of outputs, in which only one of them is "1"

# 1-to-2 (Line) Decoder

<b>A</b>	<b>D<sub>0</sub></b>	<b>D<sub>1</sub></b>
0	1	0
1	0	1

(a)

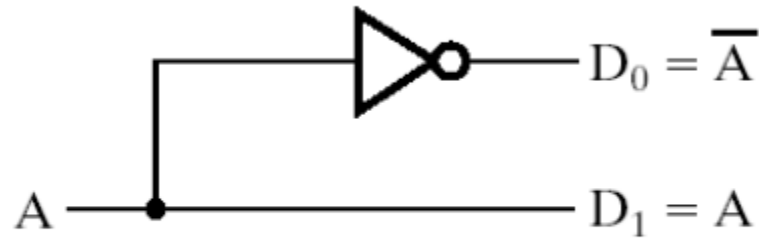

(b)

# 2-to-4 Decoder

- A 2-to-4 decoder operates according to the following truth table
  - The 2-bit input is called S1S0, and the four outputs are Q0-Q3
  - If the input is the binary number  $i$ , then output  $Q_i$  is uniquely true

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- For instance, if the input S1 S0 = 10 (decimal 2), then output Q2 is true, and Q0, Q1, Q3 are all false
- This circuit “decodes” a binary number into a “one-of-four” code

# How can you build a 2-to-4 decoder?

We have a truth table, so we can write equations for each of the four outputs (Q0-Q3)

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Equations are:

$$Q0 = S1' S0'$$


$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

# 2-to-4 Decoder

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

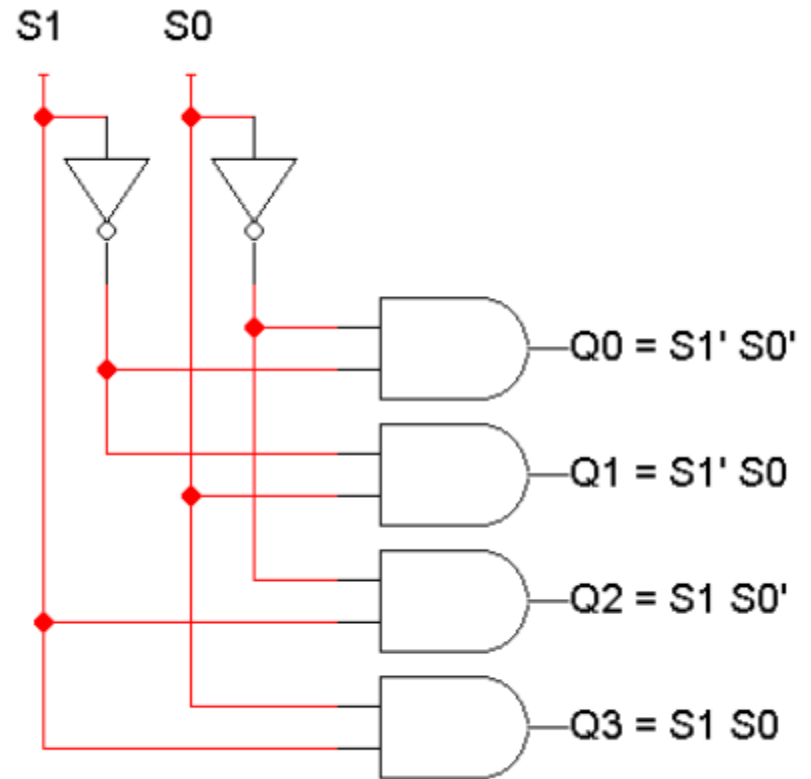



# Enable Inputs

- Many devices have an additional **enable input**, which is used to “activate” or “deactivate” the device
- For an **active-high** decoder ,
  - EN=1 activates the decoder, so it behaves as specified earlier. Exactly one of the outputs will be 1
  - EN=0 “deactivates” the decoder. By convention, that means all of the decoder’s outputs are 0
- We can include this additional input in the decoder’s truth table:

EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

# Abbreviated Truth Tables

- In the right side table, note that whenever EN=0, the outputs are always 0, **regardless** of inputs S1 and S0.



EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

- We can abbreviate the table by writing x's in the input columns for S1 and S0

EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
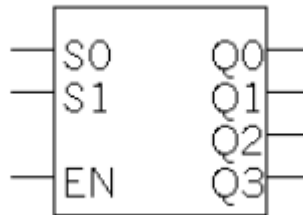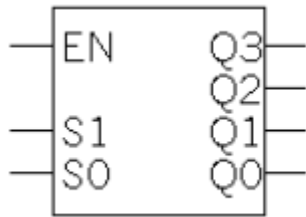
# Blocks and Abstraction

- Decoders are commonly used and it is a good idea to encapsulate them and treat them as an individual entity.
- Block diagrams** for 2-to-4 decoders are shown below.




$$\begin{aligned} Q0 &= S1' S0' \\ Q1 &= S1' S0 \\ Q2 &= S1 S0' \\ Q3 &= S1 S0 \end{aligned}$$

Advantages of a decoder block :

- You can use the decoder as long as you know its truth table or equations, without knowing exactly what's inside.
- It makes diagrams simpler by hiding the internal circuitry.
- It simplifies hardware reuse. You don't have to keep rebuilding the decoder from scratch every time you need it.
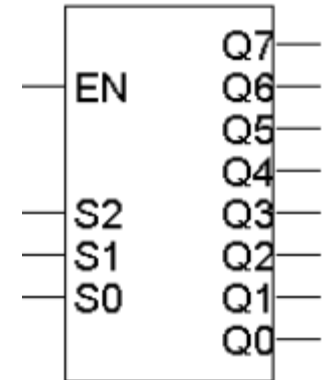
# 3-to-8 Decoder

- Larger decoders are similar. Here is a 3-to-8 decoder
  - The block symbol is on the right
  - A truth table (without EN) is below
  - Output equations are at the bottom right
- Again, only one output is true for any input combination



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q0 = S2' S1' S0'$$

$$Q1 = S2' S1' S0$$

$$Q2 = S2' S1 S0'$$

$$Q3 = S2' S1 S0$$

$$Q4 = S2 S1' S0'$$

$$Q5 = S2 S1' S0$$

$$Q6 = S2 S1 S0'$$

$$Q7 = S2 S1 S0$$

# When the decoder is used?

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$Q0 = S1' S0'$$

$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**
  - For each of the input combinations, exactly one output is true
  - Each output equation contains all of the input variables
  - These properties hold for all sizes of decoders
- Arbitrary functions can be implemented with decoders. If a sum of minterms equation for a function is given, a decoder (a minterm generator) is used to implement that function

# Decoder based Addition operation

- Let's make a circuit that adds three 1-bit inputs X, Y and Z
- We will need two bits to represent the total; let's call them C and S, for "carry" and "sum." Note that C and S are two separate functions of the same inputs X, Y and Z
- Here are a truth table and sum-of-minterms equations for C and S

$0 + 1 + 1 = 10$  →



X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

←  $1 + 1 + 1 = 11$

$C(X,Y,Z) = \sum m(3,5,6,7)$   
 $S(X,Y,Z) = \sum m(1,2,4,7)$

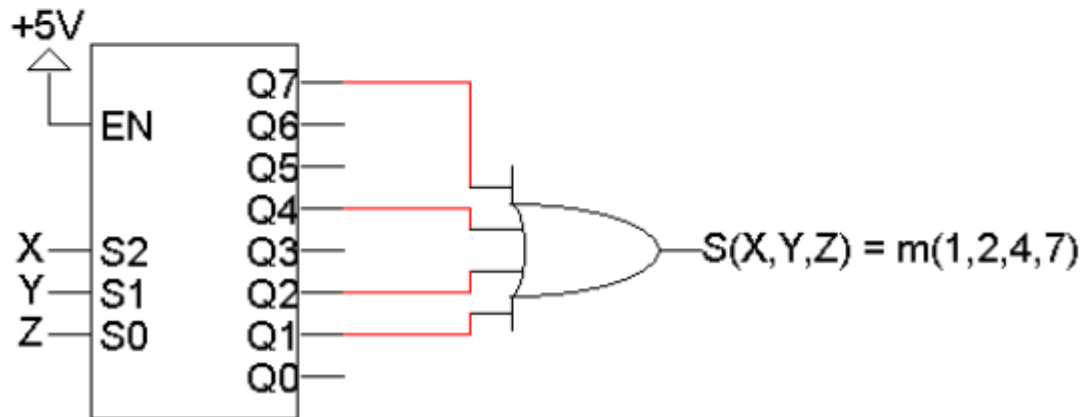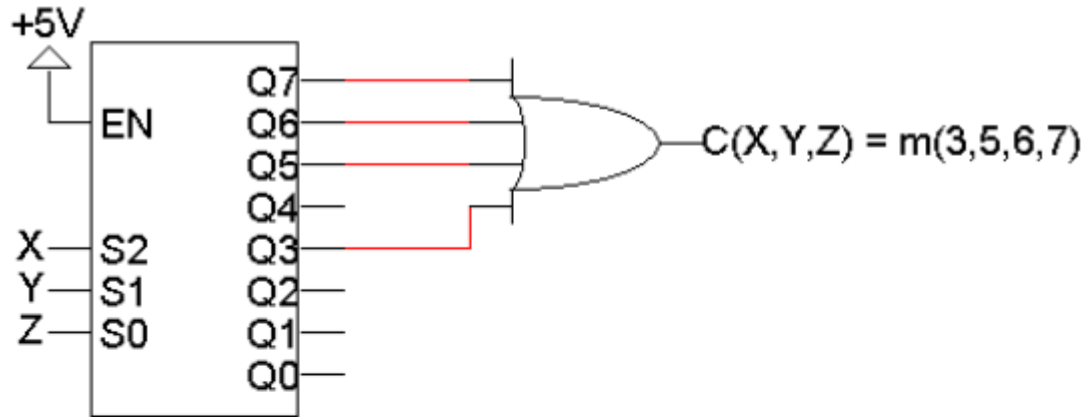
# Decoder based Addition operation cont.

- Here, two 3-to-8 decoders implement C and S as sums of minterms.


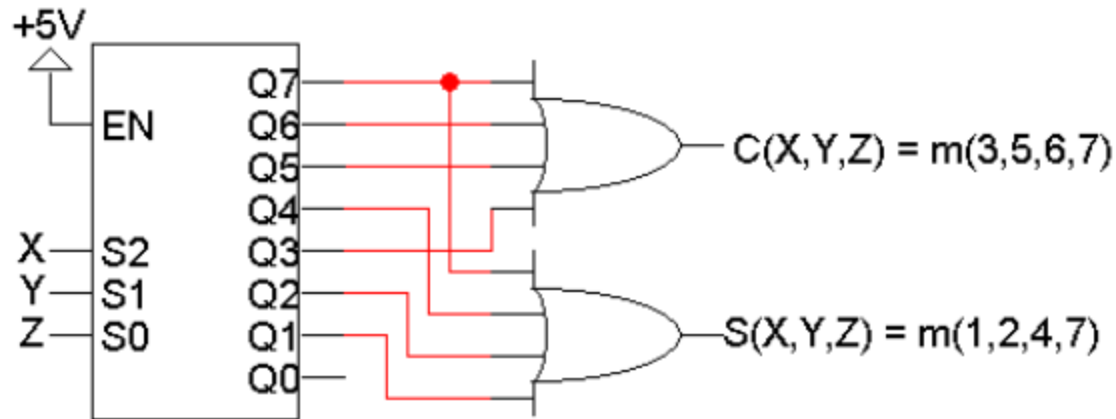
# Decoder based Addition operation cont.

- Since the two functions C and S both have the same inputs, we could use just one decoder instead of two.





# Building a 3-to-8 decoder

- You could build a 3-to-8 decoder directly from the truth table and equations below, just like how we built the 2-to-4 decoder
- Another way to design a decoder is to break it into smaller pieces
- Notice some patterns in the table below:
  - When  $S_2 = 0$ , outputs  $Q_0$ - $Q_3$  are generated as in a 2-to-4 decoder
  - When  $S_2 = 1$ , outputs  $Q_4$ - $Q_7$  are generated as in a 2-to-4 decoder

$S_2$	$S_1$	$S_0$	$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q_0 = S_2' S_1' S_0' = m_0$$

$$Q_1 = S_2' S_1' S_0 = m_1$$

$$Q_2 = S_2' S_1 S_0' = m_2$$

$$Q_3 = S_2' S_1 S_0 = m_3$$

$$Q_4 = S_2 S_1' S_0' = m_4$$


$$Q_5 = S_2 S_1' S_0 = m_5$$

$$Q_6 = S_2 S_1 S_0' = m_6$$

$$Q_7 = S_2 S_1 S_0 = m_7$$
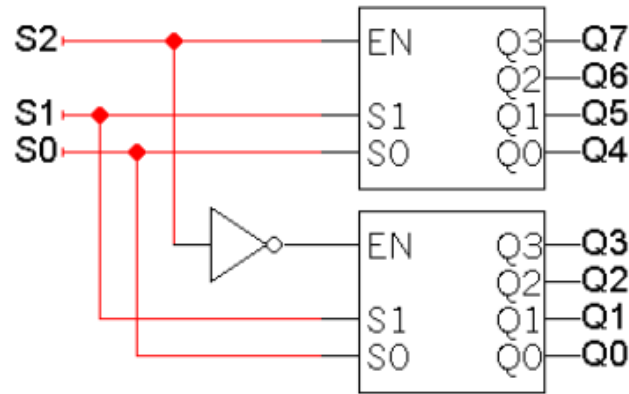
# Building a 3-to-8 decoder cont.

- You can use enable inputs to string decoders together. Here's a 3-to-8 decoder constructed from two 2-to-4 decoders:




S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Be careful not to confuse the “inner” inputs and outputs of the 2-to-4 decoders with the “outer” inputs and outputs of the 3-to-8 decoder (which are in boldface)
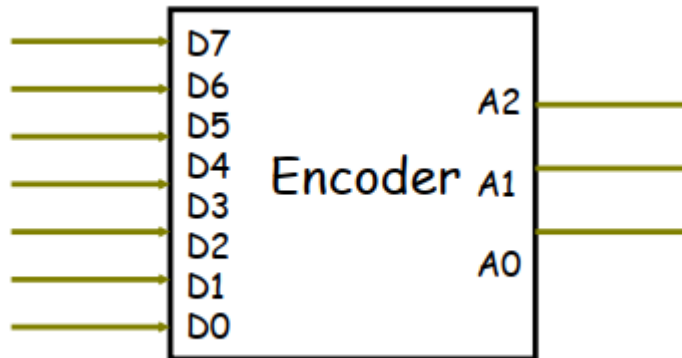
# Encoder

- An encoder is a digital function that performs the inverse operation of a decoder
- **Octal-to-Binary Encoder:** This encoder has eight inputs, one for each of the octal digits, and three outputs that generate the corresponding binary number
- - Only one input can have the value of 1 at any given time



# Octal-to-Binary Encoder

**Truth Table for Octal-to-Binary Encoder**

Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7,$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$



# Priority Encoder

- A priority encoder is a combinational circuit that implements a priority function
- Octal-to-Binary: If more than one input is active simultaneously, the output produces an incorrect combination
- Priority Encoder: If two or more inputs are active simultaneously, the input having the highest priority takes precedence

**Truth Table of Priority Encoder**

Inputs				Outputs		
D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>1</sub>	A <sub>0</sub>	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

# 4 Input Priority Encoder

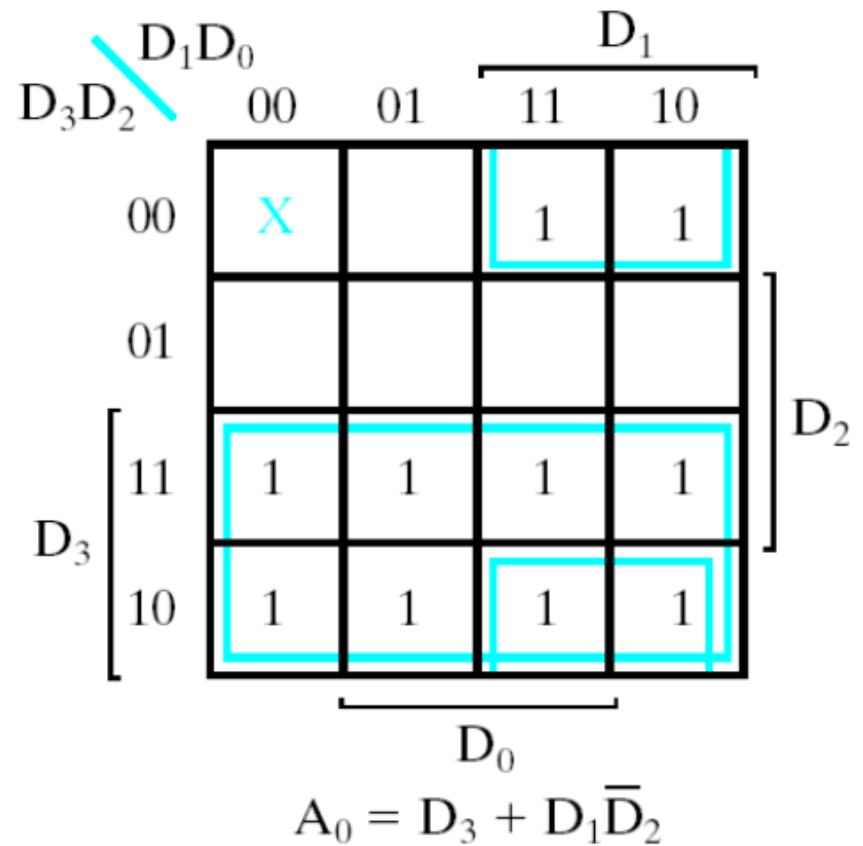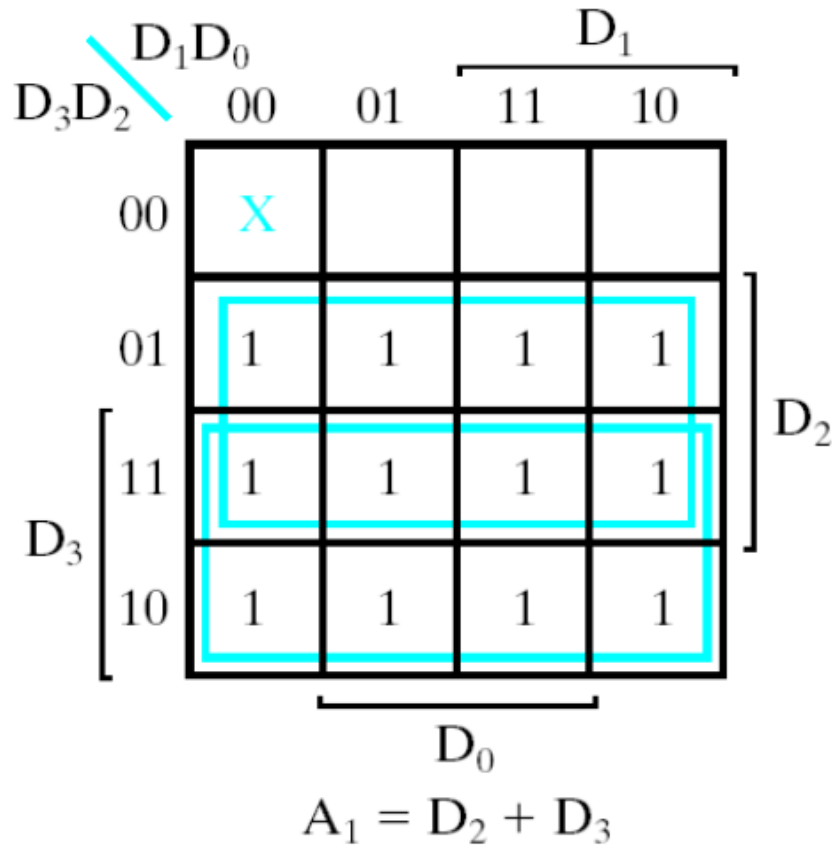

# 4 Input Priority Encoder Circuit

